

# EE 671 VLSI Design

## Course Project 1

Team 39

Jay Mehta 22B1281  
Vatsal Melwani 22B0396  
Jainam Ravani 22B1242  
Amol Pagare 22B3971

September 15, 2024

## Contents

<b>1</b>	<b>Cell 1 - BUF</b>	<b>3</b>
1.1	Circuit Diagram and MOS Sizing . . . . .	3
1.2	Layout . . . . .	4
1.3	PEX Netlist . . . . .	4
1.4	DRC and LVS Check . . . . .	5
1.4.1	DRC Check: . . . . .	5
1.4.2	LVS Check: . . . . .	5
1.5	Waveforms . . . . .	6
1.5.1	Rise and Fall Time . . . . .	6
1.5.2	Propagation Delay . . . . .	6
1.6	Input Capacitances . . . . .	7
1.7	Timing Tables . . . . .	7
1.8	Power Tables . . . . .	7
<b>2</b>	<b>Cell 2 - DFXTP</b>	<b>9</b>
2.1	Circuit Diagram and MOS sizing . . . . .	9
2.2	Layout . . . . .	10
2.3	PEX Netlist . . . . .	10
2.4	DRC and LVS Check . . . . .	13
2.4.1	DRC Check: . . . . .	13
2.4.2	LVS Check: . . . . .	13
2.5	Waveforms . . . . .	14
2.5.1	Setup Time . . . . .	14
2.5.2	Hold Time . . . . .	14
2.5.3	Rise Time . . . . .	15
2.5.4	Fall Time . . . . .	15
2.5.5	Propagation Delay . . . . .	16
2.6	Input Capacitances . . . . .	17
2.7	Timing Table . . . . .	17
2.8	Power Tables . . . . .	18

<b>3</b>	<b>Cell 3 - NOR2B</b>	<b>19</b>
3.1	Circuit Diagram and MOS Sizing . . . . .	19
3.2	Layout . . . . .	20
3.3	PEX Netlist . . . . .	20
3.4	DRC and LVS Check . . . . .	21
	3.4.1 DRC Check: . . . . .	21
	3.4.2 LVS Check: . . . . .	22
3.5	Waveforms . . . . .	22
	3.5.1 Rise Time . . . . .	22
	3.5.2 Fall Time . . . . .	23
	3.5.3 Propagation Delay . . . . .	23
3.6	Input Capacitances . . . . .	24
3.7	Timing Tables . . . . .	24
3.8	Power Tables . . . . .	25
<b>4</b>	<b>Contributions</b>	<b>27</b>

# 1 Cell 1 - BUF

## CIRCUIT DIAGRAM AND MOS SIZING

 


Figure 1: Circuit Diagram of Buffer

Index	Type of MOS	W ( $\mu\text{m}$ )	L ( $\mu\text{m}$ )
X0	n-MOS	0.42	0.15
X1	n-MOS	0.42	0.15
X2	p-MOS	1.27	0.15
X3	p-MOS	0.42	0.15

Table 1: MOSFET Parameters

# LAYOUT

Following is the layout, with the dimensions mentioned in the terminal for magic.

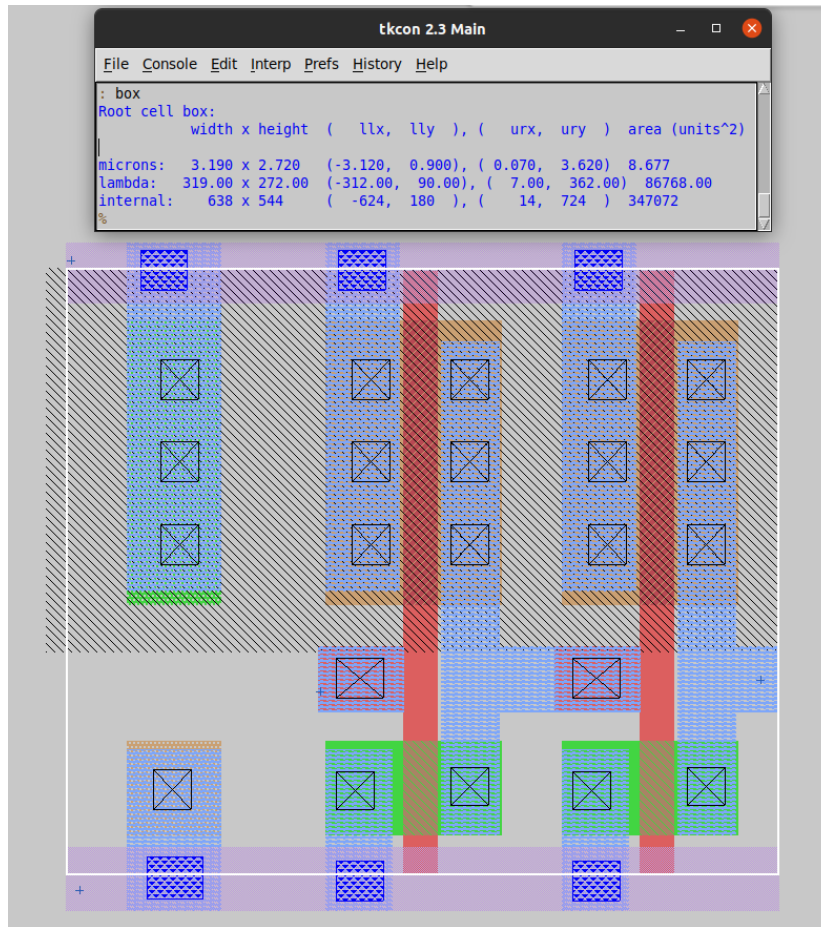


Figure 2: Layout for Buffer with dimensions

# PEX NETLIST

Following is the netlist with parasitics generated using magic.

\* NGSPICE file created from NOR.ext - technology: sky130A

```
.subckt BUFX1 gnd A Z vdd
X0 a_n294_216# A Gnd Gnd sky130_fd_pr__nfet_01v8 ad=0.1218 pd=1.42 as=0.147
ps=1.54 w=0.42 l=0.15
X1 Z a_n294_216# Vdd Vdd sky130_fd_pr__pfet_01v8 ad=0.3683 pd=3.12 as=0.4445
ps=3.24 w=1.27 l=0.15
X2 Z a_n294_216# Gnd Gnd sky130_fd_pr__nfet_01v8 ad=0.1218 pd=1.42 as=0.147
ps=1.54 w=0.42 l=0.15
X3 a_n294_216# A Vdd Vdd sky130_fd_pr__pfet_01v8 ad=0.3683 pd=3.12 as=0.4445
ps=3.24 w=1.27 l=0.15
C0 A a_n294_216# 0.07097f
C1 Z a_n294_216# 0.060637f
C2 Vdd A 0.116746f
C3 Z Vdd 0.117794f
C4 Vdd a_n294_216# 0.300854f
C5 Z Gnd 0.168793f
C6 A Gnd 0.214202f
C7 Vdd Gnd 0.999662f
```

C8 a\_n294\_216# Gnd 0.332985f  
.ends

## DRC AND LVS CHECK

### 1.4.1 DRC Check:

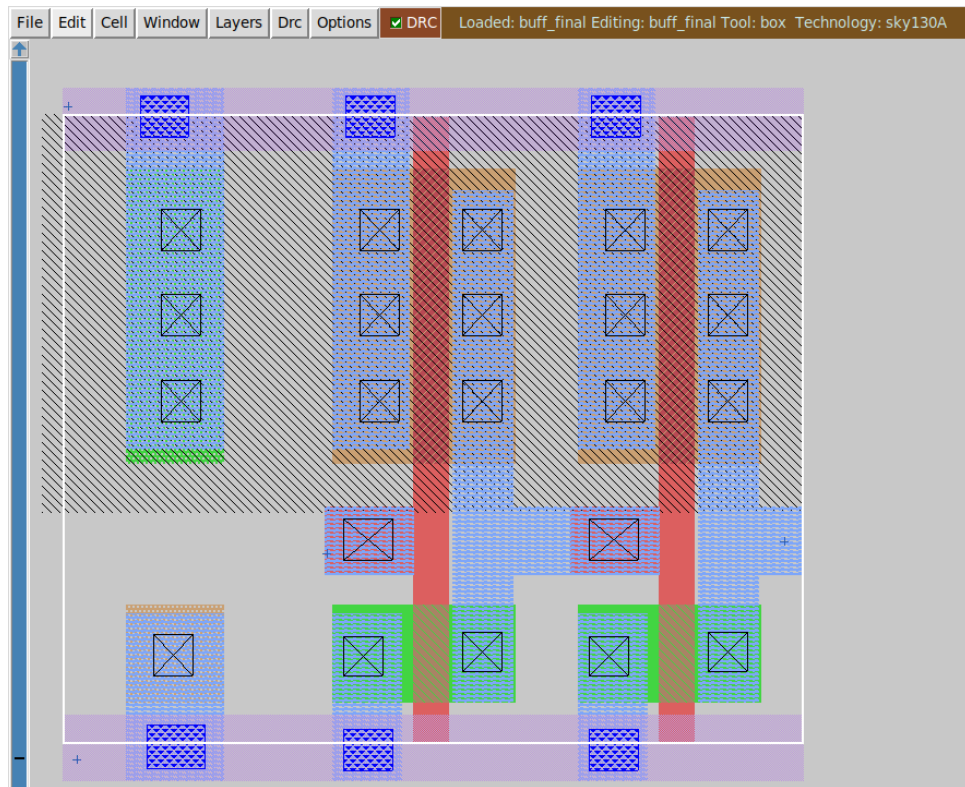


Figure 3: DRC Clean Proof

### 1.4.2 LVS Check:

```
jainam@jainam-HP-Laptop-15s-fq5xxx:~/new_pdk_sky/course_project1/buff_final$ netgen -batch lvs "buff_final.spice" "buff_schematic.spice" /usr/local/share/pdk/sky130A/libs.tech/netgen/sky130A_setup.tcl | tail -n 22
Contents of circuit 1: Circuit: 'buff_final.spice'
Circuit buff_final.spice contains 13 device instances.
  Class: sky130_fd_pr__nfet_01v8 instances:  2
  Class: c                instances:  9
  Class: sky130_fd_pr__pfet_01v8 instances:  2
Circuit contains 5 nets.
Contents of circuit 2: Circuit: 'buff_schematic.spice'
Circuit buff_schematic.spice contains 13 device instances.
  Class: sky130_fd_pr__nfet_01v8 instances:  2
  Class: c                instances:  9
  Class: sky130_fd_pr__pfet_01v8 instances:  2
Circuit contains 5 nets.

Circuit 1 contains 13 devices, Circuit 2 contains 13 devices.
Circuit 1 contains 5 nets,   Circuit 2 contains 5 nets.

Final result:
Circuits match uniquely.
Logging to file "comp.out" disabled
LVS Done.
```

Figure 4: LVS Clean Proof

# WAVEFORMS

## 1.5.1 Rise and Fall Time

 


Figure 5: Rise and Fall Time

## 1.5.2 Propagation Delay

 


Figure 6: Propagation delay

## INPUT CAPACITANCES

Input Pins	Rise Cap (fF)	Fall Cap (fF)	Average Cap (fF)
A	2.317	2.281	2.30

Table 2: Input Pin Capacitances

## TIMING TABLES

	10 ps	100 ps	1000 ps
0.5 fF	14.5 ps	14.7 ps	30.0
10 fF	67.4 ps	67.3 ps	73.7
100 fF	592.2 ps	592.2 ps	592.8

Table 3: Output Rise Transitions (in ns) [Input slew vs output capacitance]. Related pin A

	10 ps	100 ps	1000 ps
0.5 fF	14.5 ps	14.7 ps	27.8
10 fF	72.7 ps	72.8 ps	79.3
100 fF	641.3 ps	641.2 ps	642.2

Table 4: Output Fall Transitions (in ns) [Input slew vs output capacitance]. Related pin A

	10 ps	100 ps	1000 ps
0.5 fF	47.1 ps	65.6 ps	145.1
10 fF	87.6 ps	106.1 ps	196.8
100 fF	446.0 ps	464.6 ps	556.4

Table 5: Cell Rise Delay (in ns) [Input slew vs output capacitance]. Related pin A

	10 ps	100 ps	1000 ps
0.5 fF	46.1 ps	67.0 ps	157.6
10 fF	96.0 ps	117.6 ps	217.3
100 fF	532.0 ps	554.1 ps	656.3

Table 6: Cell Fall Delay (in ns) [Input slew vs output capacitance]. Related pin A

## POWER TABLES

Condition (A)	Power (nW)
0	0.11634
1	0.11634

Table 7: Static Power (all possible input combinations of A)

	10 ps	100 ps	1000 ps
0.5 fF	88.39	24.05	5.59
10 fF	162.00	96.08	35.71
100 fF	170.29	173.12	36.79

Table 8: Dynamic Power Table (i) Rise Power (in uW) [Input slew vs output capacitance]. Related pin A

	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	94.92	66.04	15.22
10 fF	96.00	67.36	15.60
100 fF	120.96	68.81	6.50

Table 9: Dynamic Power Table (ii) Fall Power (in uW) [Input slew vs output capacitance]. Related pin A



## 2 Cell 2 - DFXTP

### CIRCUIT DIAGRAM AND MOS SIZING

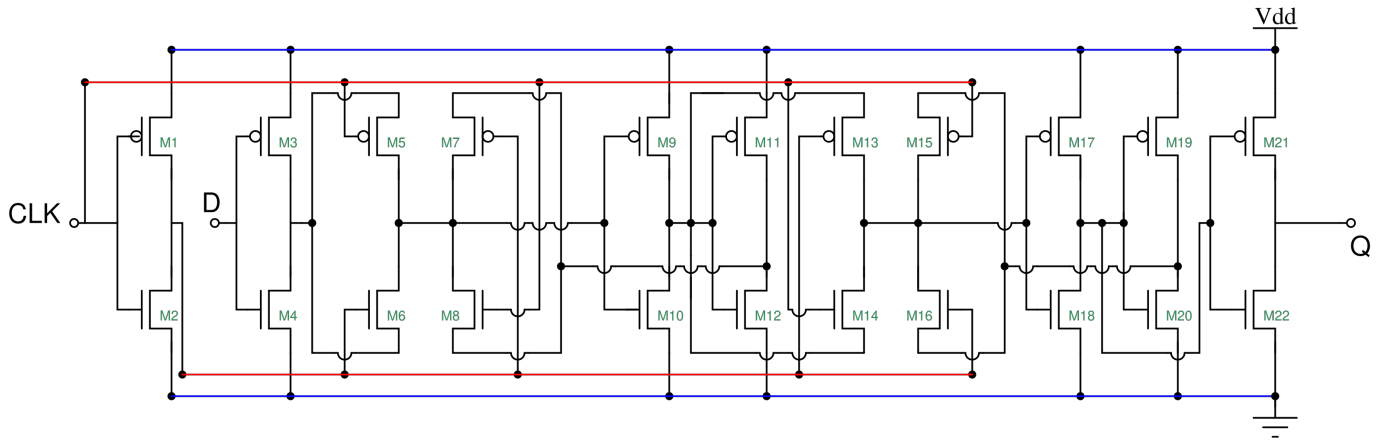


Figure 7: Circuit Diagram of Positive Edge Data Flip-Flop

Index	Type of MOS	W ( $\mu\text{m}$ )	L ( $\mu\text{m}$ )
X0	n-MOS	0.42	0.15
X1	n-MOS	0.42	0.15
X2	p-MOS	1.27	0.15
X3	n-MOS	0.42	0.15
X4	p-MOS	1.27	0.15
X5	n-MOS	0.42	0.15
X6	p-MOS	1.27	0.15
X7	p-MOS	1.27	0.15
X8	n-MOS	0.42	0.15
X9	n-MOS	0.42	0.15
X10	n-MOS	0.42	0.15
X11	n-MOS	0.42	0.15
X12	n-MOS	0.42	0.15
X13	p-MOS	1.27	0.15
X14	p-MOS	1.27	0.15
X15	n-MOS	0.42	0.15
X16	n-MOS	0.42	0.15
X17	p-MOS	1.27	0.15
X18	p-MOS	1.27	0.15
X19	p-MOS	1.27	0.15
X20	p-MOS	1.27	0.15
X21	p-MOS	1.27	0.15

Table 10: MOSFET Parameters

(NOTE: The indexes of MOSFETS are according to that generated in the pex file)

## LAYOUT

Following is the layout, with the dimensions mentioned in the terminal for magic. Note, the terminal shows 2.71um, but in reality it's 2.72um only. It shows 2.71 because of the grid length quantization constraints:

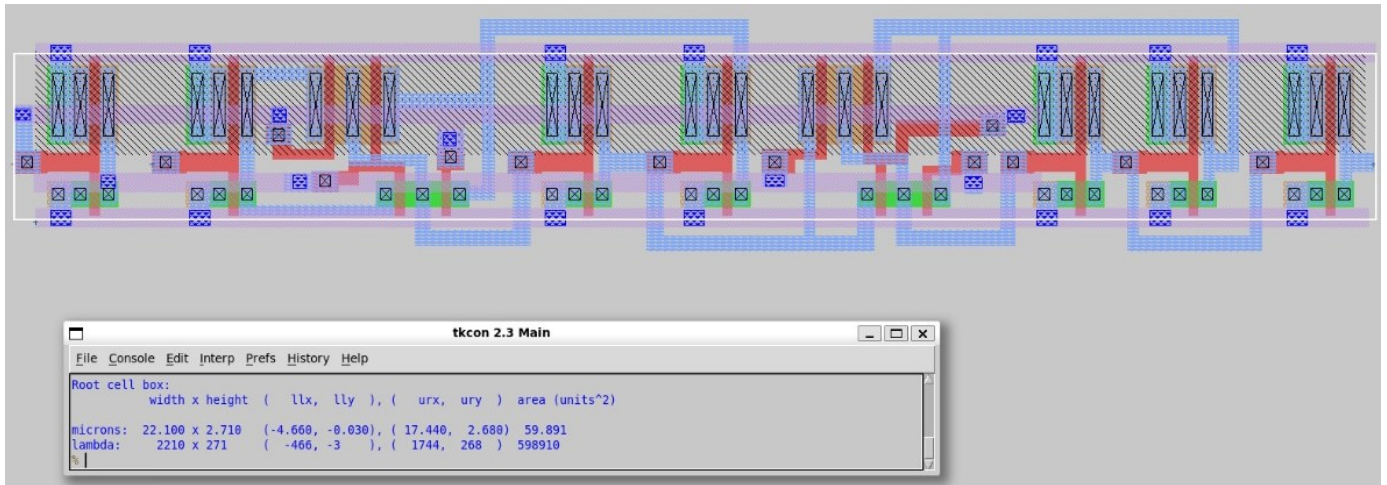


Figure 8: Layout for DFF with dimensions

## PEX NETLIST

```
* NGSPICE file created from dff.ext - technology: sky130A
.lib /usr/local/share/pdk/sky130A/libs.tech/ngspice/sky130.lib.spice tt
.subckt dff D clk Q vss vdd
X0 a_927_120# a_1272_18# vss vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.44 as=0.126
ps=1.44 w=0.42 l=0.15
**devattr s=1260,144 d=1260,144
X1 a_927_120# a_n327_18# a_852_120# vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.44
as=0.126 ps=1.02 w=0.42 l=0.15
**devattr s=1260,102 d=1260,144
X2 a_n327_18# clk vdd vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=3.14 as=0.381
ps=3.14 w=1.27 l=0.15
**devattr s=3810,314 d=3810,314
X3 a_852_120# clk a_474_18# vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.02 as=0.126
ps=1.44 w=0.42 l=0.15
**devattr s=1260,144 d=1260,102
X4 a_927_120# clk a_852_120# vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=3.14 as=0.381
ps=1.87 w=1.27 l=0.15
**devattr s=3810,187 d=3810,314
X5 a_n102_18# D vss vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.44 as=0.126
ps=1.44 w=0.42 l=0.15
**devattr s=1260,144 d=1260,144
X6 a_1272_18# a_852_120# vdd vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=3.14 as=0.381
ps=3.14 w=1.27 l=0.15
**devattr s=3810,314 d=3810,314
X7 a_n102_18# D vdd vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=3.14 as=0.381
ps=3.14 w=1.27 l=0.15
**devattr s=3810,314 d=3810,314
X8 a_n327_18# clk vss vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.44 as=0.126
ps=1.44 w=0.42 l=0.15
**devattr s=1260,144 d=1260,144
X9 a_1272_18# a_852_120# vss vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.44 as=0.126
```

```

ps=1.44 w=0.42 l=0.15
**devattr s=1260,144 d=1260,144
X10 a_54_120# a_n327_18# a_n102_18# vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.02
as=0.126 ps=1.44 w=0.42 l=0.15
**devattr s=1260,144 d=1260,102
X11 a_129_120# clk a_54_120# vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.44 as=0.126
ps=1.02 w=0.42 l=0.15
**devattr s=1260,102 d=1260,144
X12 a_474_18# a_54_120# vss vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.44 as=0.126
ps=1.44 w=0.42 l=0.15
**devattr s=1260,144 d=1260,144
X13 a_129_120# a_474_18# vdd vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=3.14 as=0.381
ps=3.14 w=1.27 l=0.15
**devattr s=3810,314 d=3810,314
X14 a_927_120# a_1272_18# vdd vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=3.14 as=0.381
ps=3.14 w=1.27 l=0.15
**devattr s=3810,314 d=3810,314
X15 a_129_120# a_474_18# vss vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.44 as=0.126
ps=1.44 w=0.42 l=0.15
**devattr s=1260,144 d=1260,144
X16 Q a_1272_18# vss vss sky130_fd_pr__nfet_01v8 ad=0.126 pd=1.44 as=0.126
ps=1.44 w=0.42 l=0.15
**devattr s=1260,144 d=1260,144
X17 a_852_120# a_n327_18# a_474_18# vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=1.87
as=0.381 ps=3.14 w=1.27 l=0.15
**devattr s=3810,314 d=3810,187
X18 a_474_18# a_54_120# vdd vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=3.14 as=0.381
ps=3.14 w=1.27 l=0.15
**devattr s=3810,314 d=3810,314
X19 Q a_1272_18# vdd vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=3.14 as=0.381
ps=3.14 w=1.27 l=0.15
**devattr s=3810,314 d=3810,314
X20 a_129_120# a_n327_18# a_54_120# vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=3.14
as=0.381 ps=1.87 w=1.27 l=0.15
**devattr s=3810,187 d=3810,314
X21 a_54_120# clk a_n102_18# vdd sky130_fd_pr__pfet_01v8 ad=0.381 pd=1.87 as=0.381
ps=3.14 w=1.27 l=0.15
**devattr s=3810,314 d=3810,187
C0 Q vdd 0.121471f
C1 clk a_852_120# 0.149059f
C2 D clk 0.039876f
C3 clk a_927_120# 0.167326f
C4 a_852_120# a_927_120# 0.16653f
C5 clk a_474_18# 0.120984f
C6 a_852_120# a_474_18# 0.168917f
C7 clk a_1272_18# 0.002125f
C8 a_927_120# a_474_18# 1.16e-19
C9 clk a_n327_18# 1.04126f
C10 a_852_120# a_1272_18# 0.064204f
C11 a_1272_18# a_927_120# 0.142062f
C12 a_n327_18# a_852_120# 0.215813f
C13 D a_n327_18# 0.052048f
C14 a_n327_18# a_927_120# 0.108192f

```

C15 a\_1272\_18# a\_474\_18# 5.4e-19  
C16 a\_n327\_18# a\_474\_18# 0.261757f  
C17 Q clk 1.06e-19  
C18 a\_n327\_18# a\_1272\_18# 0.002477f  
C19 a\_n102\_18# a\_129\_120# 4.41e-20  
C20 vdd a\_129\_120# 0.620602f  
C21 Q a\_927\_120# 0.002157f  
C22 vdd a\_n102\_18# 0.185954f  
C23 a\_54\_120# a\_129\_120# 0.230387f  
C24 Q a\_1272\_18# 0.04166f  
C25 a\_54\_120# a\_n102\_18# 0.140363f  
C26 vdd a\_54\_120# 0.179205f  
C27 Q a\_n327\_18# 6.22e-20  
C28 clk a\_129\_120# 0.259362f  
C29 a\_852\_120# a\_129\_120# 1.44e-19  
C30 D a\_129\_120# 2.9e-20  
C31 clk a\_n102\_18# 0.214076f  
C32 clk vdd 1.94632f  
C33 a\_927\_120# a\_129\_120# 0.009133f  
C34 vdd a\_852\_120# 0.170864f  
C35 D a\_n102\_18# 0.044298f  
C36 D vdd 0.142067f  
C37 vdd a\_927\_120# 0.68069f  
C38 a\_474\_18# a\_129\_120# 0.13261f  
C39 clk a\_54\_120# 0.146185f  
C40 vdd a\_474\_18# 0.352639f  
C41 D a\_54\_120# 4.4e-20  
C42 a\_n327\_18# a\_129\_120# 0.140951f  
C43 vdd a\_1272\_18# 0.466938f  
C44 a\_54\_120# a\_474\_18# 0.058552f  
C45 a\_n327\_18# a\_n102\_18# 0.196172f  
C46 vdd a\_n327\_18# 0.434253f  
C47 a\_n327\_18# a\_54\_120# 0.18053f  
C48 Q vss 0.18321f  
C49 D vss 0.281218f  
C50 clk vss 0.84449f  
C51 vdd vss 5.43907f  
C52 a\_927\_120# vss 0.494246f  
C53 a\_129\_120# vss 0.445621f  
C54 a\_n102\_18# vss 0.332164f  
C55 a\_1272\_18# vss 1.0964f  
C56 a\_852\_120# vss 0.614379f  
C57 a\_474\_18# vss 0.958008f  
C58 a\_54\_120# vss 0.635279f  
C59 a\_n327\_18# vss 2.34082f  
.ends  
.end

# DRC AND LVS CHECK

## 2.4.1 DRC Check:

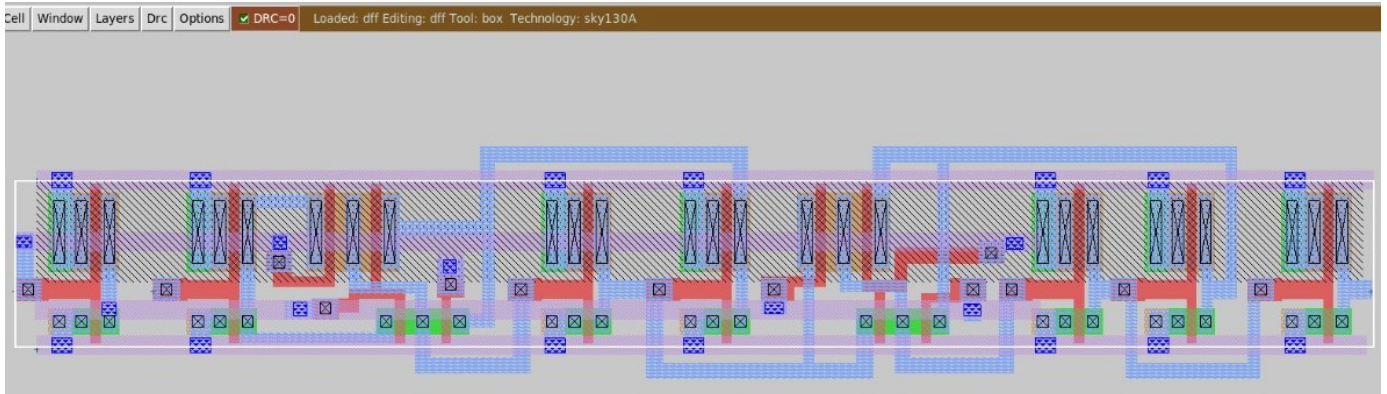


Figure 9: DRC Clean Proof

## 2.4.2 LVS Check:

```
Contents of circuit 1: Circuit: 'dff'
Circuit dff contains 22 device instances.
  Class: sky130_fd_pr__nfet_01v8 instances:  11
  Class: sky130_fd_pr__pfet_01v8 instances:  11
Circuit contains 13 nets.
Contents of circuit 2: Circuit: 'dff'
Circuit dff contains 22 device instances.
  Class: sky130_fd_pr__nfet_01v8 instances:  11
  Class: sky130_fd_pr__pfet_01v8 instances:  11
Circuit contains 13 nets.

Circuit 1 contains 22 devices, Circuit 2 contains 22 devices.
Circuit 1 contains 13 nets,    Circuit 2 contains 13 nets.

Final result:
Circuits match uniquely.
.
Logging to file "comp.out" disabled
LVS Done.
```

Figure 10: LVS Clean Proof

# WAVEFORMS

## 2.5.1 Setup Time

Rise setup time plot for input and clock skew both as 10ps (piecewise linear function was used to generate clk and D waveforms):

 


Figure 11: Setup time for 10ps slew for D and clk both

## 2.5.2 Hold Time

Fall hold time for slew as 1000ps for both input and clk(same legend as setup time plot):

 


Figure 12: Hold time for 1000ps slew for D and clk



Legend:

Red - clk

Blue - D

Yellow - Q

(legend is same for hold time plot also)

NOTE: Setup and Hold times were measured as respective differences in time of D and CLK when the levels reach 50% of the vdd value. Hence, in some of the cases, values come out to be negative for the parameters.

### 2.5.3 Rise Time

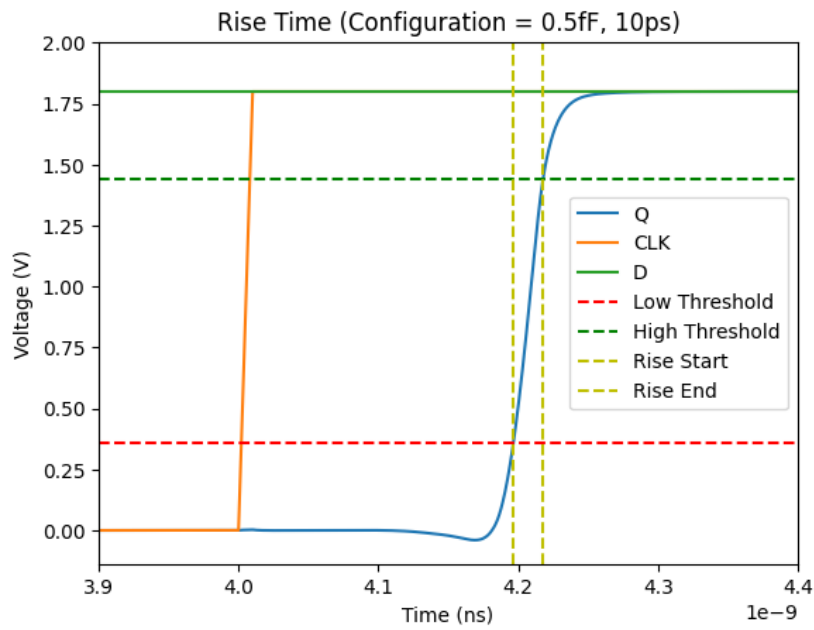


Figure 13: Rise Time

### 2.5.4 Fall Time

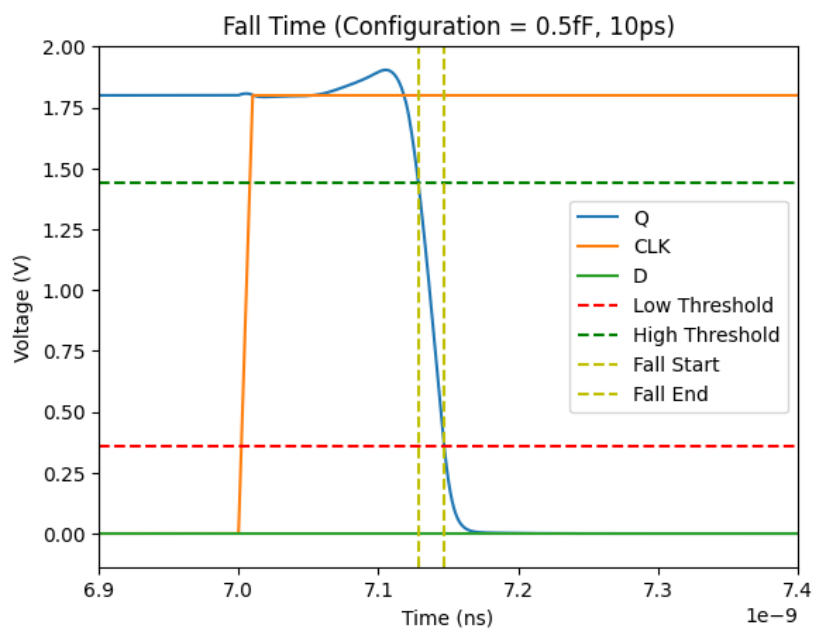


Figure 14: Fall Time

### 2.5.5 Propagation Delay

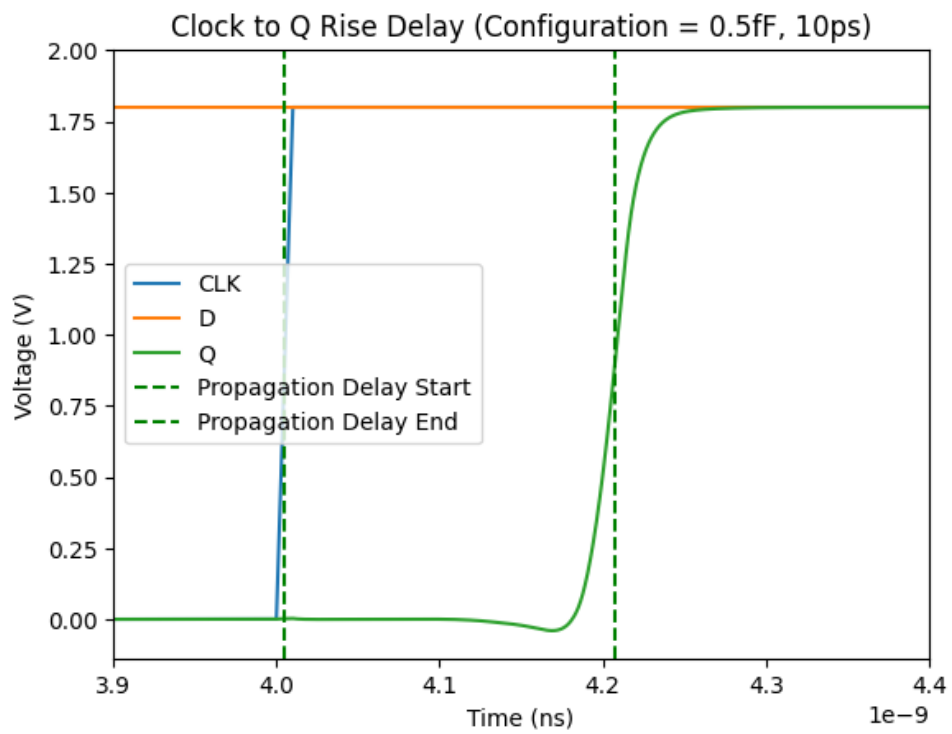


Figure 15: Propagation Delay - Rise

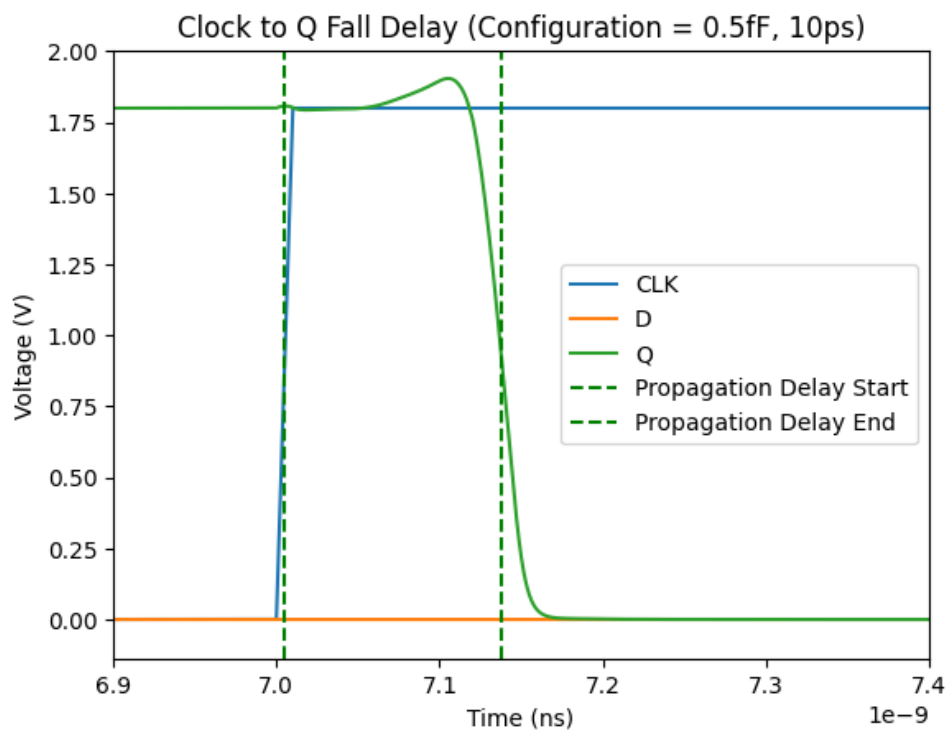


Figure 16: Propagation Delay - Fall



## INPUT CAPACITANCES

Input Pins	Rise Cap (pF)	Fall Cap (pF)	Average Cap (pF)
D	$2.4978 \times 10^{-3}$	$2.4852 \times 10^{-3}$	$2.4915 \times 10^{-3}$
CLK	$9.3546 \times 10^{-3}$	$9.3358 \times 10^{-3}$	$9.3452 \times 10^{-3}$

Table 11: Input Pin Capacitances

## TIMING TABLE

	10 ps	1000 ps
10 ps	0.115	-0.008
1000 ps	0.282	0.140

Table 12: Set-up Time Table (i) Rise Constraint (in ns) [Input slew vs CLK slew]

	10 ps	1000 ps
10 ps	0.11	0.191
1000 ps	0.28	0.353

Table 13: Set-up Time Table (ii) Fall Constraint (in ns) [Input slew vs CLK slew]

	10 ps	1000 ps
10 ps	-0.069	-0.172
1000 ps	-0.228	-0.334

Table 14: Hold Time Table (i) Rise Constraint (in ns) [Input slew vs CLK slew]

	10 ps	1000 ps
10 ps	-0.062	0.01
1000 ps	-0.212	-0.133

Table 15: Hold Time Table (ii) Fall Constraint (in ns) [Input slew vs CLK slew]

	10 ps	100 ps	1000 ps
0.5 fF	$21.15 \times 10^{-3}$	$21.15 \times 10^{-3}$	$21.1 \times 10^{-3}$
10 fF	$71.4 \times 10^{-3}$	$71.4 \times 10^{-3}$	$71.4 \times 10^{-3}$
100 fF	$592.2 \times 10^{-3}$	$592.2 \times 10^{-3}$	$592.2 \times 10^{-3}$

Table 16: Transition Time Table (i) Output Rise Transitions (in ns) [Input slew vs output capacitance].  
Related pin D:

	10 ps	100 ps	1000 ps
0.5 fF	$18.46 \times 10^{-3}$	$18.50 \times 10^{-3}$	$19.4 \times 10^{-3}$
10 fF	$75.96 \times 10^{-3}$	$75.98 \times 10^{-3}$	$76.4 \times 10^{-3}$
100 fF	$641.3 \times 10^{-3}$	$641.3 \times 10^{-3}$	$641.3 \times 10^{-3}$

Table 17: Transition Time Table (ii) Output Fall Transitions (in ns) [Input slew vs output capacitance].  
Related pin D:

	10 ps	100 ps	1000 ps
0.5 fF	202.48*10 <sup>-3</sup>	220.47*10 <sup>-3</sup>	374.8*10 <sup>-3</sup>
10 fF	249.29*10 <sup>-3</sup>	267.28*10 <sup>-3</sup>	421.6*10 <sup>-3</sup>
100 fF	608.8*10 <sup>-3</sup>	626.8*10 <sup>-3</sup>	781.2*10 <sup>-3</sup>

Table 18: CLK-to-Q Delay Time Table (i) Cell Rise Delay (in ns) [Input slew vs output capacitance]. Related pin D:

	10 ps	100 ps	1000 ps
0.5 fF	133.33*10 <sup>-3</sup>	150.97*10 <sup>-3</sup>	269.3*10 <sup>-3</sup>
10 fF	188.32*10 <sup>-3</sup>	206.02*10 <sup>-3</sup>	324.8*10 <sup>-3</sup>
100 fF	625.5*10 <sup>-3</sup>	643.2*10 <sup>-3</sup>	762.3*10 <sup>-3</sup>

Table 19: CLK-to-Q Delay Time Table (ii) Cell Fall Delay (in ns) [Input slew vs output capacitance]. Related pin D:

## POWER TABLES

Condition (CLK D)	Power (nW)
00	380.91*10 <sup>-3</sup>
01	380.95*10 <sup>-3</sup>
10	490.58*10 <sup>-3</sup>
11	490.59*10 <sup>-3</sup>

Table 20: Static Power (all possible input combinations of CLK and D)

	10 ps	100 ps	1000 ps
0.5 fF	115.83*10 <sup>3</sup>	84.32*10 <sup>3</sup>	30.13*10 <sup>3</sup>
10 fF	198.62*10 <sup>3</sup>	143.17*10 <sup>3</sup>	56.03*10 <sup>3</sup>
100 fF	232.94*10 <sup>3</sup>	195.45*10 <sup>3</sup>	142.36*10 <sup>3</sup>

Table 21: Dynamic Power Table (i) Rise Power (in nW) [Clk slew vs output capacitance]. Related pin D:

	10 ps	100 ps	1000 ps
0.5 fF	112.37*10 <sup>3</sup>	69.24*10 <sup>3</sup>	20.52*10 <sup>3</sup>
10 fF	108.85*10 <sup>3</sup>	76.71*10 <sup>3</sup>	20.33*10 <sup>3</sup>
100 fF	46.39*10 <sup>3</sup>	42.29*10 <sup>3</sup>	18.65*10 <sup>3</sup>

Table 22: Dynamic Power Table (ii) Fall Power (in nW) [Clk slew vs output capacitance]. Related pin D:

NOTE: We have changed the slew for clk rather than input while calculating the dynamic power as the transition in the state takes place at the rising edge of the clk and not the edge of input. Hence, it makes sense to change the slew of the rising edge of the clk while calculating the dynamic power.

### 3 Cell 3 - NOR2B

#### CIRCUIT DIAGRAM AND MOS SIZING

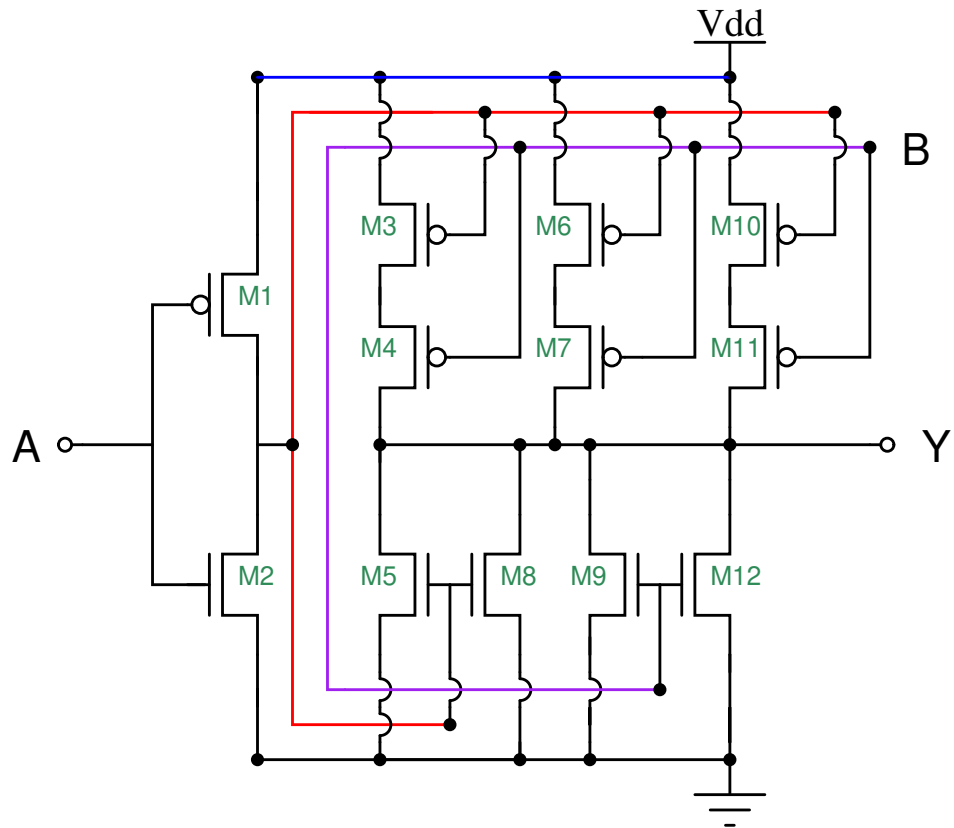


Figure 17: Circuit Diagram of NOR

Index	Type of MOS	W ( $\mu\text{m}$ )	L ( $\mu\text{m}$ )
xn1	p-MOS	1.27	0.15
xn2	p-MOS	1.27	0.15
xn3	p-MOS	0.66	0.15
xn4	p-MOS	1.27	0.15
xn5	p-MOS	1.27	0.15
xn6	p-MOS	0.66	0.15
xn7	n-MOS	0.42	0.15
xn8	n-MOS	0.42	0.15
xn9	n-MOS	0.42	0.15
xn10	n-MOS	0.42	0.15
x11	p-MOS	1.27	0.15
x12	n-MOS	0.42	0.15

Table 23: MOSFET Parameters

# LAYOUT

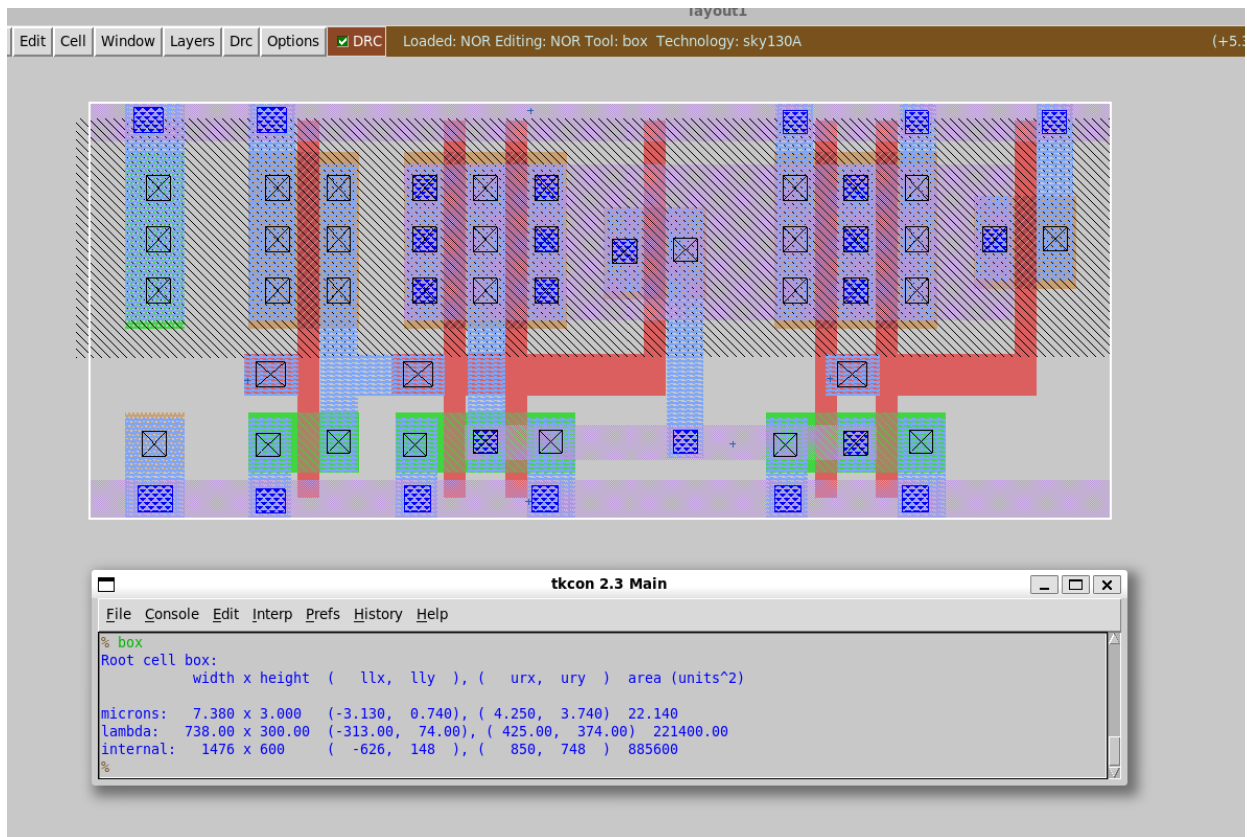


Figure 18: Layout for NOR with dimensions

## PEX NETLIST

\* NGSPICE file created from NOR.ext - technology: sky130A

```
X0 a_n170_422# B vdd vdd sky130_fd_pr__pfet_01v8 ad=0.295215 pd=2.611438 as=0.38995
ps=3.233244 w=1.27 l=0.15
X1 a_n294_216# A vss vss sky130_fd_pr__nfet_01v8 ad=0.1218 pd=1.42 as=0.147
ps=1.54 w=0.42 l=0.15
X2 Y a_n294_216# a_n170_422# vdd sky130_fd_pr__pfet_01v8 ad=0.222131
pd=1.992312 as=0.295215 ps=2.611438 w=1.27 l=0.15
X3 vss B Y vss sky130_fd_pr__nfet_01v8 ad=0.147 pd=1.54 as=0.0609
ps=0.71 w=0.42 l=0.15
X4 a_n170_422# a_n294_216# Y vdd sky130_fd_pr__pfet_01v8 ad=0.295215
pd=2.611438 as=0.222131 ps=1.992312 w=1.27 l=0.15
X5 vdd B a_n170_422# vdd sky130_fd_pr__pfet_01v8 ad=0.202651 pd=1.680268 as=0.153419
ps=1.357125 w=0.66 l=0.15
X6 Y B vss vss sky130_fd_pr__nfet_01v8 ad=0.0609 pd=0.71 as=0.147
ps=1.54 w=0.42 l=0.15
X7 Y a_n294_216# vss vss sky130_fd_pr__nfet_01v8 ad=0.0609 pd=0.71 as=0.147
ps=1.54 w=0.42 l=0.15
X8 a_n294_216# A vdd vdd sky130_fd_pr__pfet_01v8 ad=0.3683 pd=3.12 as=0.38995
ps=3.233244 w=1.27 l=0.15
X9 vdd B a_n170_422# vdd sky130_fd_pr__pfet_01v8 ad=0.38995 pd=3.233244 as=0.295215
ps=2.611438 w=1.27 l=0.15
X10 vss a_n294_216# Y vss sky130_fd_pr__nfet_01v8 ad=0.147 pd=1.54 as=0.0609
ps=0.71 w=0.42 l=0.15
```

```

X11 Y a_n294_216# a_n170_422# vdd sky130_fd_pr__pfet_01v8 ad=0.115438
pd=1.035375 as=0.153419 ps=1.357125 w=0.66 l=0.15
C0 vdd a_n294_216# 0.390535f
C1 B a_n170_422# 0.097495f
C2 a_n170_422# a_n294_216# 0.186942f
C3 A a_n294_216# 0.07097f
C4 vdd Y 0.075827f
C5 B a_n294_216# 0.016201f
C6 a_n170_422# Y 0.494385f
C7 a_n170_422# vdd 1.01649f
C8 A Y 4.72e-19
C9 vdd A 0.11508f
C10 a_n170_422# A 0.003227f
C11 B Y 0.05308f
C12 B vdd 0.283403f
C13 Y a_n294_216# 0.147628f
C14 B vss 0.417836f
C15 Y vss 0.643651f
C16 A vss 0.214244f
C17 vdd vss 2.12895f
C18 a_n170_422# vss 0.186014f
C19 a_n294_216# vss 0.555133f

```

## DRC AND LVS CHECK

### 3.4.1 DRC Check:

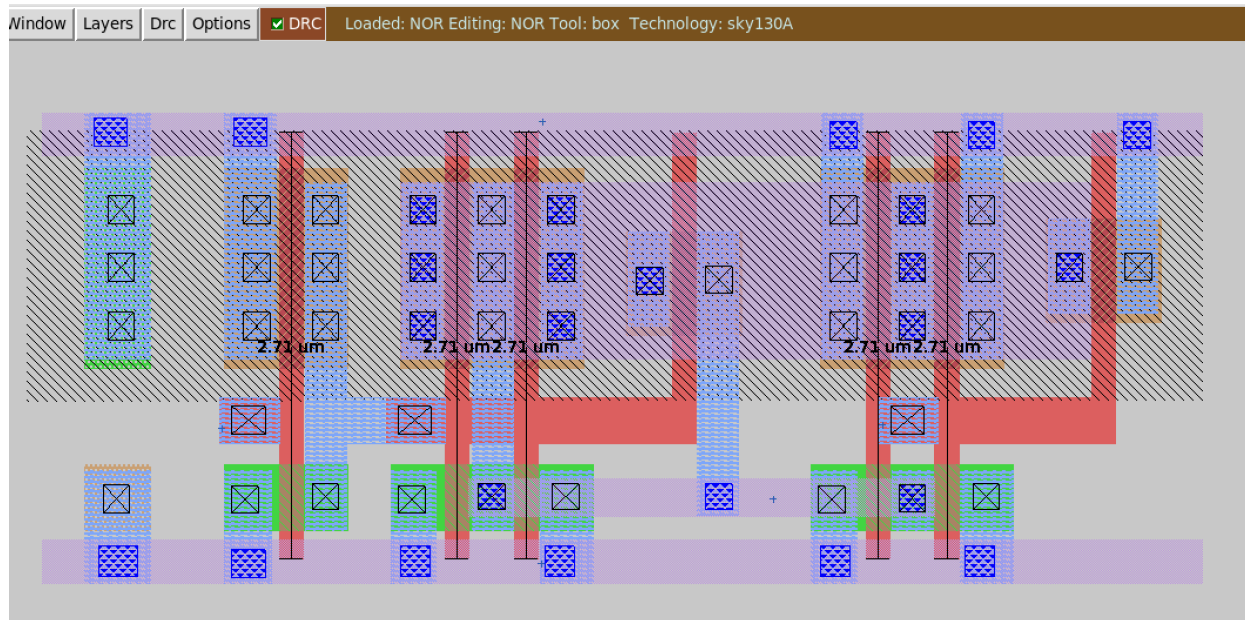


Figure 19: DRC Clean Proof

### 3.4.2 LVS Check:

```
amol_18@DESKTOP-Q99KTQ7:/mnt/d/VLSI_Design/Course_Project_All_Files/Final_NOR$ netgen -
batch lvs "norx1_layout.spice NOR1" "norx1_schematic.spice NORs" /usr/local/share/pdk/s
ky130A/libs.tech/netgen/sky130A_setup.tcl | tail -n 22
Contents of circuit 1: Circuit: 'NOR1'
Circuit NOR1 contains 6 device instances.
  Class: sky130_fd_pr__nfet_01v8 instances: 3
  Class: sky130_fd_pr__pfet_01v8 instances: 3
Circuit contains 7 nets.
Contents of circuit 2: Circuit: 'NORs'
Circuit NORs contains 6 device instances.
  Class: sky130_fd_pr__nfet_01v8 instances: 3
  Class: sky130_fd_pr__pfet_01v8 instances: 3
Circuit contains 7 nets.

Circuit 1 contains 6 devices, Circuit 2 contains 6 devices.
Circuit 1 contains 7 nets, Circuit 2 contains 7 nets.

No more changes can be made to series/parallel networks.
No more changes can be made to series/parallel networks.

Final result:
Circuits match uniquely.
.
Logging to file "comp.out" disabled
LVS Done.
amol_18@DESKTOP-Q99KTQ7:/mnt/d/VLSI_Design/Course_Project_All_Files/Final_NOR$
```

Figure 20: LVS Clean Proof

## WAVEFORMS

### 3.5.1 Rise Time

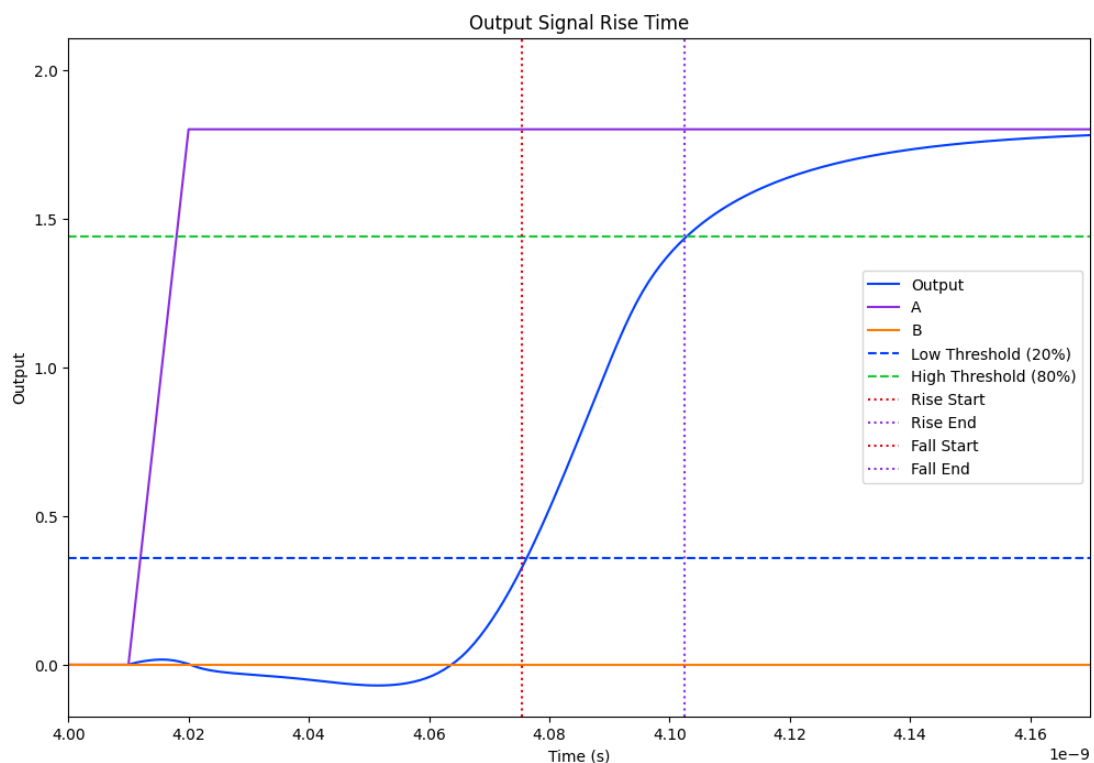


Figure 21: Rise Time

3.5.2 Fall Time

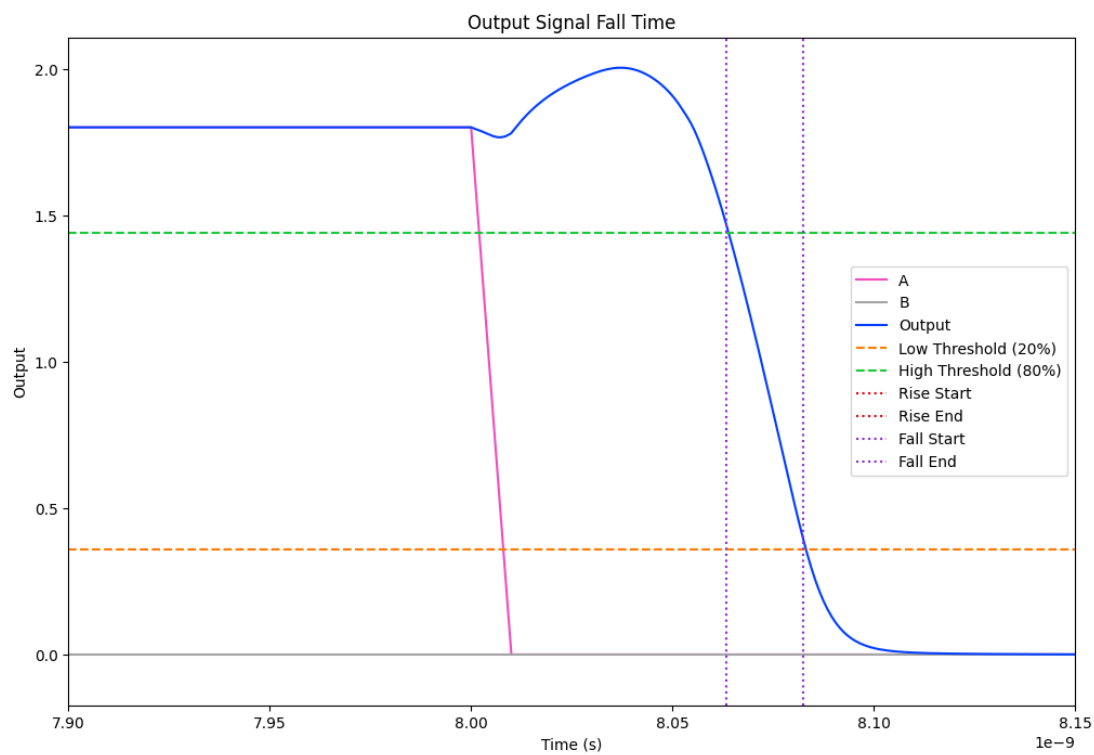


Figure 22: Fall Time

3.5.3 Propagation Delay

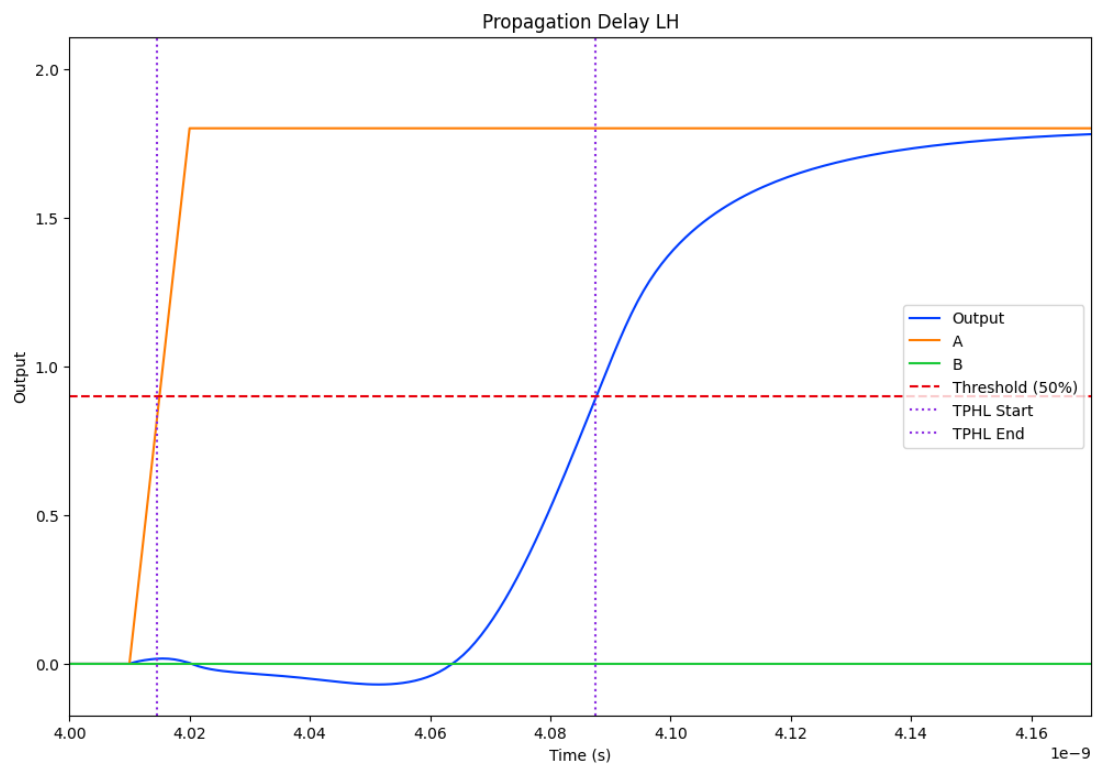


Figure 23: LH Propagation delay

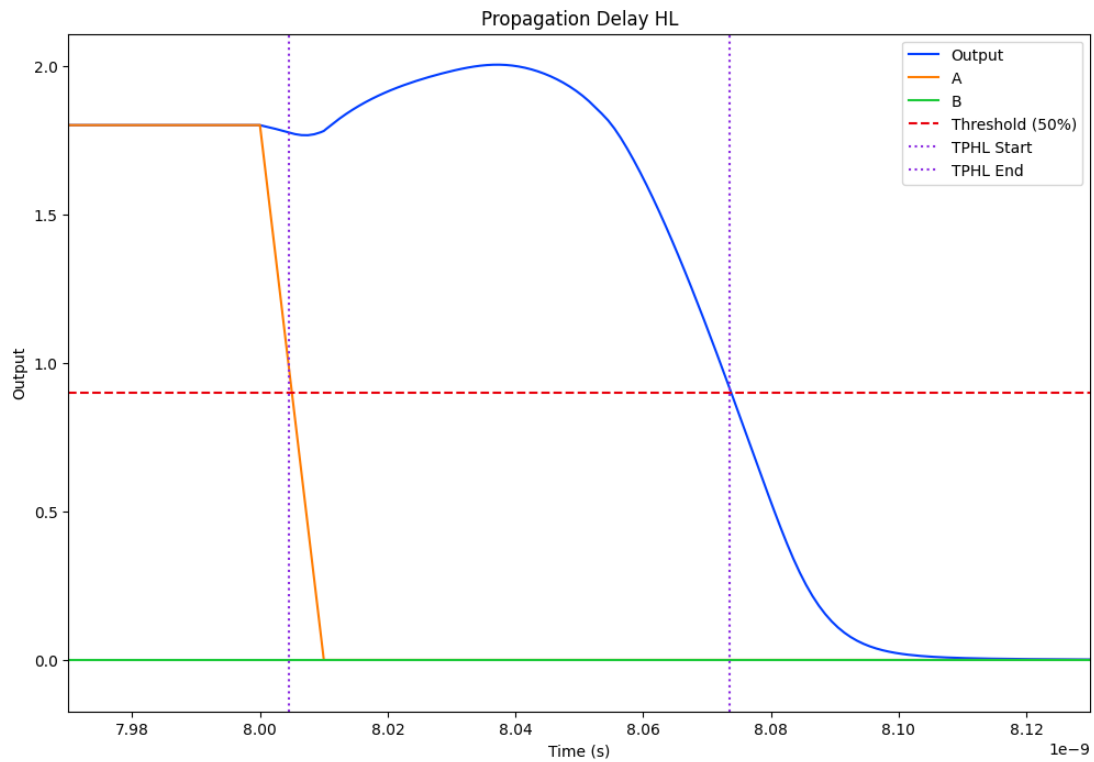


Figure 24: HL Propagation delay

## INPUT CAPACITANCES

Input Pins	Rise Cap (pF)	Fall Cap (pF)	Average Cap (pF)
A	$2.24 \times 10^{-3}$	$2.32 \times 10^{-3}$	$2.28 \times 10^{-3}$
B	$5.6 \times 10^{-3}$	$5.5 \times 10^{-3}$	$5.55 \times 10^{-3}$

Table 24: Input Pin Capacitances

## TIMING TABLES

	10 ps	100 ps	1000 ps
0.5 fF	$27 \times 10^{-3}$	$27 \times 10^{-3}$	$42 \times 10^{-3}$
10 fF	$68 \times 10^{-3}$	$68.99 \times 10^{-3}$	$79 \times 10^{-3}$
100 fF	$484 \times 10^{-3}$	$484.99 \times 10^{-3}$	$483.99 \times 10^{-3}$

Table 25: Output Rise Transitions (in ns) [Input slew vs output capacitance]. Related pin A

	10 ps	100 ps	1000 ps
0.5 fF	$24 \times 10^{-3}$	$26.86 \times 10^{-3}$	$89 \times 10^{-3}$
10 fF	$68 \times 10^{-3}$	$69 \times 10^{-3}$	$138.99 \times 10^{-3}$
100 fF	$484 \times 10^{-3}$	$485 \times 10^{-3}$	$502.86 \times 10^{-3}$

Table 26: Output Rise Transitions (in ns) [Input slew vs output capacitance]. Related pin B



	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	$19 \times 10^{-3}$	$19 \times 10^{-3}$	$34 \times 10^{-3}$
10 fF	$47 \times 10^{-3}$	$47 \times 10^{-3}$	$59 \times 10^{-3}$
100 fF	$329 \times 10^{-3}$	$328.99 \times 10^{-3}$	$329.99 \times 10^{-3}$

Table 27: Output Fall Transitions (in ns) [Input slew vs output capacitance]. Related pin A

	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	$26.99 \times 10^{-3}$	$27.99 \times 10^{-3}$	$96 \times 10^{-3}$
10 fF	$57.99 \times 10^{-3}$	$56 \times 10^{-3}$	$146 \times 10^{-3}$
100 fF	$340 \times 10^{-3}$	$342 \times 10^{-3}$	$433 \times 10^{-3}$

Table 28: Output Fall Transitions (in ns) [Input slew vs output capacitance]. Related pin B

	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	$73 \times 10^{-3}$	$92 \times 10^{-3}$	$201.99 \times 10^{-3}$
10 fF	$106.99 \times 10^{-3}$	$124.99 \times 10^{-3}$	$244 \times 10^{-3}$
100 fF	$402 \times 10^{-3}$	$421 \times 10^{-3}$	$538.99 \times 10^{-3}$

Table 29: Cell Rise Delay (in ns) [Input slew vs output capacitance]. Related pin A

	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	$37.86 \times 10^{-3}$	$57.86 \times 10^{-3}$	$116 \times 10^{-3}$
10 fF	$70.86 \times 10^{-3}$	$90.86 \times 10^{-3}$	$198 \times 10^{-3}$
100 fF	$364 \times 10^{-3}$	$385.86 \times 10^{-3}$	$561.86 \times 10^{-3}$

Table 30: Cell Rise Delay (in ns) [Input slew vs output capacitance]. Related pin B

	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	$68.99 \times 10^{-3}$	$90.99 \times 10^{-3}$	$221 \times 10^{-3}$
10 fF	$97.99 \times 10^{-3}$	$120 \times 10^{-3}$	$257 \times 10^{-3}$
100 fF	$318.99 \times 10^{-3}$	$340.99 \times 10^{-3}$	$483 \times 10^{-3}$

Table 31: Cell Fall Delay (in ns) [Input slew vs output capacitance]. Related pin A

	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	$32.99 \times 10^{-3}$	$51.99 \times 10^{-3}$	$140.99 \times 10^{-3}$
10 fF	$58.99 \times 10^{-3}$	$77 \times 10^{-3}$	$203.99 \times 10^{-3}$
100 fF	$279.99 \times 10^{-3}$	$298.99 \times 10^{-3}$	$505.99 \times 10^{-3}$

Table 32: Cell Fall Delay (in ns) [Input slew vs output capacitance]. Related pin B

## POWER TABLES

<b>Condition (AB)</b>	<b>Power (nW)</b>
00	0.623
01	0.618
10	0.986
11	0.616

Table 33: Static Power (all possible input combinations of AB)

	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	294.30*10 <sup>3</sup>	209.58*10 <sup>3</sup>	77.93*10 <sup>3</sup>
10 fF	428.53*10 <sup>3</sup>	369.81*10 <sup>3</sup>	143.51*10 <sup>3</sup>
100 fF	677.91*10 <sup>3</sup>	477.18*10 <sup>3</sup>	302.44*10 <sup>3</sup>

Table 34: Dynamic Power Table (i) Rise Power (in nW) [Input slew vs output capacitance]. Related pin A

	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	334.29*10 <sup>3</sup>	252.24*10 <sup>3</sup>	66.84*10 <sup>3</sup>
10 fF	551.45*10 <sup>3</sup>	389.55*10 <sup>3</sup>	124.34*10 <sup>3</sup>
100 fF	708.68*10 <sup>3</sup>	466.52*10 <sup>3</sup>	319.09*10 <sup>3</sup>

Table 35: Dynamic Power Table (i) Rise Power (in nW) [Input slew vs output capacitance]. Related pin B

	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	339.58*10 <sup>3</sup>	245.51*10 <sup>3</sup>	74.68*10 <sup>3</sup>
10 fF	593.35*10 <sup>3</sup>	433.21*10 <sup>3</sup>	137.05*10 <sup>3</sup>
100 fF	1059.69*10 <sup>3</sup>	739.64*10 <sup>3</sup>	421.02*10 <sup>3</sup>

Table 36: Dynamic Power Table (ii) Fall Power (in nW) [Input slew vs output capacitance]. Related pin A

	<b>10 ps</b>	<b>100 ps</b>	<b>1000 ps</b>
0.5 fF	877.52*10 <sup>3</sup>	409.89*10 <sup>3</sup>	68.15*10 <sup>3</sup>
10 fF	1102.91*10 <sup>3</sup>	612.16*10 <sup>3</sup>	126.78*10 <sup>3</sup>
100 fF	1431.54*10 <sup>3</sup>	1005.32*10 <sup>3</sup>	347.11*10 <sup>3</sup>

Table 37: Dynamic Power Table (ii) Fall Power (in nW) [Input slew vs output capacitance]. Related pin B

## 4 Contributions

- Jay
  1. NOR layout design
  2. Power Calculations, Input Capacitances, Rise Time, Fall Time and Propagation Delays for DFF
- Vatsal
  1. DFF layout design
  2. Setup and Hold time calculations for DFF
- Jainam
  1. Buffer layout design
  2. Complete characterisation of Buffer
- Amol
  1. NOR layout design
  2. Complete characterisation of NOR gate